

R20

SET-I

7 R

**CMR TECHNICAL CAMPUS
UGC AUTONOMOUS**

**B.Tech - IV Semester, Regular End Examinations, July-2022
Analog and Digital Electronics (20EC402PC)
(Common to CSM & CSD)**

Time: 3 Hours

Max. Marks: 70

**Answer Any Five Questions
All Questions Carry Equal Marks .**

5 X 14 = 70 Marks

1. a. With the help of a neat circuit diagram, explain the working of an series biased clipper. [7M]
b. Explain the characteristics, working & Volt Ampere Characteristics of Tunnel diodes, [7M]
2. a. Explain the construction, working and characteristics of Photo Diode? [7M]
b. State and prove the clamping circuit theorem? [7M]
3. a. Explain the operation of FET with its characteristics and explain the different regions in transfer characteristics? [7M]
b. Define pinch-off voltage and trans conductance in field effect transistors? [7M]
4. a. Explain how a FET can be made to act as a voltage variable resistor? [7M]
b. Bring out the differences between FET and MOSFET. Draw the circuit diagram of CS JFET amplifier? [7M]
5. a. Explain the working of CMOS as an inverter? [7M]
b. Draw the basic TTL logic NAND gate and explain it. [7M]
6. a. Design a two-input NOR and two-input NAND using DTL logic. [7M]
b. Compare different logic families [7M]
7. a. Summarize the Boolean function $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15) + d(w, x, y, z) = \Sigma(0, 2, 5)$ [7M]
b. Use a multiplexer having three data select inputs to solve the logic for the function $F = \Sigma(0, 1, 2, 3, 4, 10, 11, 14, 15)$ [7M]
8. a. Explain the state reduction, state assignment with an example. [7M]
b. Design a 4-bit BCD Ripple Counter by using T-FF? [7M]

**CMR TECHNICAL CAMPUS
UGC AUTONOMOUS**

B. Tech. IV Semester Supply End Examinations, February-2024

Analog and Digital Electronics

Common to CSM, CSD, AIML, CSG

Time: 3 Hours

Max. Marks: 70

Note

- i. This Question paper contains Part- A and Part- B.
- ii. All the Questions in Part A are to be answered compulsorily.
- iii. All Questions from Part B are to be answered with internal choice among them.

PART-A

10 X 02 = 20 Marks

| | | Marks | CO | BL |
|----|---|--------------|-----------|-----------|
| 1. | a | 2 | CO1 | L1 |
| | b | 2 | CO1 | L1 |
| | c | 2 | CO2 | L1 |
| | d | 2 | CO2 | L1 |
| | e | 2 | CO3 | L3 |
| | f | 2 | CO3 | L1 |
| | g | 2 | CO4 | L1 |
| | h | 2 | CO4 | L1 |
| | i | 2 | CO5 | L2 |
| | j | 2 | CO5 | L1 |

PART- B

5 X 10 = 50 Marks

| | | Marks | CO | BL |
|----|--|--------------|-----------|-----------|
| 2. | From the Energy band diagram explain the V-I characteristics of a tunnel Diode. List the applications of tunnel diode. | 10 | CO1 | L2 |
| | OR | | | |
| 3 | a | 5 | CO1 | L2 |
| | b | 5 | CO1 | L2 |
| 4 | a | 5 | CO2 | L2 |
| | b | 5 | CO2 | L2 |

OR

- 5 a Discuss the theoretical operation CS FET amplifier. 5 CO2 L1
 b Explain the construction & operation of a P-channel MOSFET in enhancement and depletion modes with the help of static drain characteristics and transfer characteristics? 5 CO2 L2
- 6 a Perform The Following Conversions 5 CO3 L3
 i) $(AB)_{16} = ()_{10}$
 ii) $(123)_8 = ()_{10}$
 iii) $(346)_8 = ()_2$
 iv) $(100011001)_2 = ()_{16}$
 b Show that the dual of the Exclusive – OR is equal to its complement. 5 CO3 L2
- OR
- 7 a Describe the operation of DTL NAND Gate 5 CO3 L2
 b Realize 2-input OR gates using CMOS logic and then explain its operation with the help of functional table. 5 CO3 L2
- 8 a Minimize the following expression using K-map and realize using NAND Gates. $F(A,B,C,D) = \sum m(0,1,2,9,11) + d(8,10,14,15)$. 5 CO4 L2
 b Simplify the following Boolean expressions to a minimum number of literals 5 CO4 L3
 (i) $ABC + A'B + ABC'$ (ii) $xy + x(wz + wz')$
- OR
- 9 a Design and explain a 4-bit binary parallel Adder/Subtractor. 5 CO4 L3
 b Define a multiplexer? Draw a 2:1 multiplexer for the function $f(x,y,z) = \sum(0,2,3,5,7)$ 5 CO4 L3
- 10 a Explain the operation SR flip flop. Explain its truth table. 5 CO5 L2
 b Find the characteristic equation for: 5 CO5 L1
 i) T flip-flop ii) D flip-flop
- OR
- 11 a Design Mod-10 Synchronous counter using T flip-flop. 5 CO5 L3
 b Design a 3 bit Ripple counter. 5 CO5 L3